

IN THIS ISSUE...

COVER ARTICLE

A Standards Lab Grade 20-Bit DAC with 0.1ppm/°C Drift 1

Jim Williams, Jim Brubaker, Patrick Copley, Josh Guerrero and Florin Oprescu

Issue Highlights 2

LTC® in the News 2

DESIGN FEATURES

LT®1766: 1.5A Converter Runs Directly from 60V DC 5

Mark W. Marosek

Digitally Programmable Low Noise Filter/Gain Block Requires No External Parts 7

Max W. Hauser

No Latency Delta-Sigma ADC Techniques for Optimized Performance 10

Michael K. Mayes

High Power Desktop CCFL Controller Enables Wide Dimming Ratios while Maximizing Lamp Lifetime 15

Rich Philpott

LT1815: 220MHz, 1500V/μs Amplifier Saves Space and Power 18

Kris Lokere

Constant-Current DC/DC Converter Drives White LEDs with 80% Efficiency 21

Bryan Legates

LT1880 SOT-23 Op Amp Saves Board Space in Precision Applications 23

Glen Brisebois

DESIGN IDEAS

..... 25-37

(complete listing on page 25)

New Device Cameos 38

Design Tools 39

Sales Offices 40



A Standards Lab Grade 20-Bit DAC with 0.1ppm/°C Drift

The Dedicated Art of Digitizing One Part Per Million

by Jim Williams, Jim Brubaker, Patrick Copley, Josh Guerrero and Florin Oprescu

Introduction

Significant progress in high precision, instrumentation grade D-to-A conversion has recently occurred. Ten years ago 12-bit D-to-A converters (DACs) were considered premium devices. Today, 16-bit DACs are available and increasingly common in system design. These are true precision devices with less than 1LSB linearity error and 1ppm/°C drift. Nonetheless, there are DAC applications that require even higher performance. Automatic test equipment, instruments, calibration apparatus, laser trimmers, medical electronics and other applications often require DAC accuracy beyond 16 bits. 18-bit DACs have been produced in circuit assembly form, although they are expensive and require frequent calibration. 20 and

even 23+ (0.1ppm!) bit DACs are represented by manually switched Kelvin-Varley dividers. These devices, although amazingly accurate, are large, slow and extremely costly. Their use is normally restricted to standards labs. A useful development would be a practical, 20-bit (1ppm) DAC that is easily constructed and does not require frequent calibration.¹

20-Bit DAC Architecture

Figure 1 diagrams the architecture of a 20-bit (1ppm) DAC. This scheme is based on the availability of a true 1ppm analog-to-digital converter with scale and zero drifts below 0.02ppm/°C. This device, the LTC®2400, is used as a feedback element in a digitally corrected loop to realize a 20-bit DAC.

continued on page 3

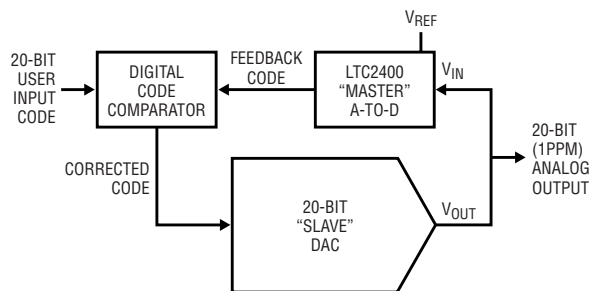


Figure 1. Conceptual, loop-based 20-bit DAC: digital comparison allows A-to-D to correct DAC errors. The LTC2400 A-to-D's low uncertainty characteristics permit 1ppm output accuracy.

¹ LTC and LT are registered trademarks of Linear Technology Corporation. Adaptive Power, Burst Mode, C-Load, DirectSense, FilterCAD, Hot Swap, LinearView, Micropower SwitcherCAD, Multimode Dimming, No Latency ΔΣ, No R_{SENSE}, Operational Filter, OPTI-LOOP, Over-The-Top, PolyPhase, PowerSOT, SwitcherCAD and UltraFast are trademarks of Linear Technology Corporation. Other product names may be trademarks of the companies that manufacture the products.

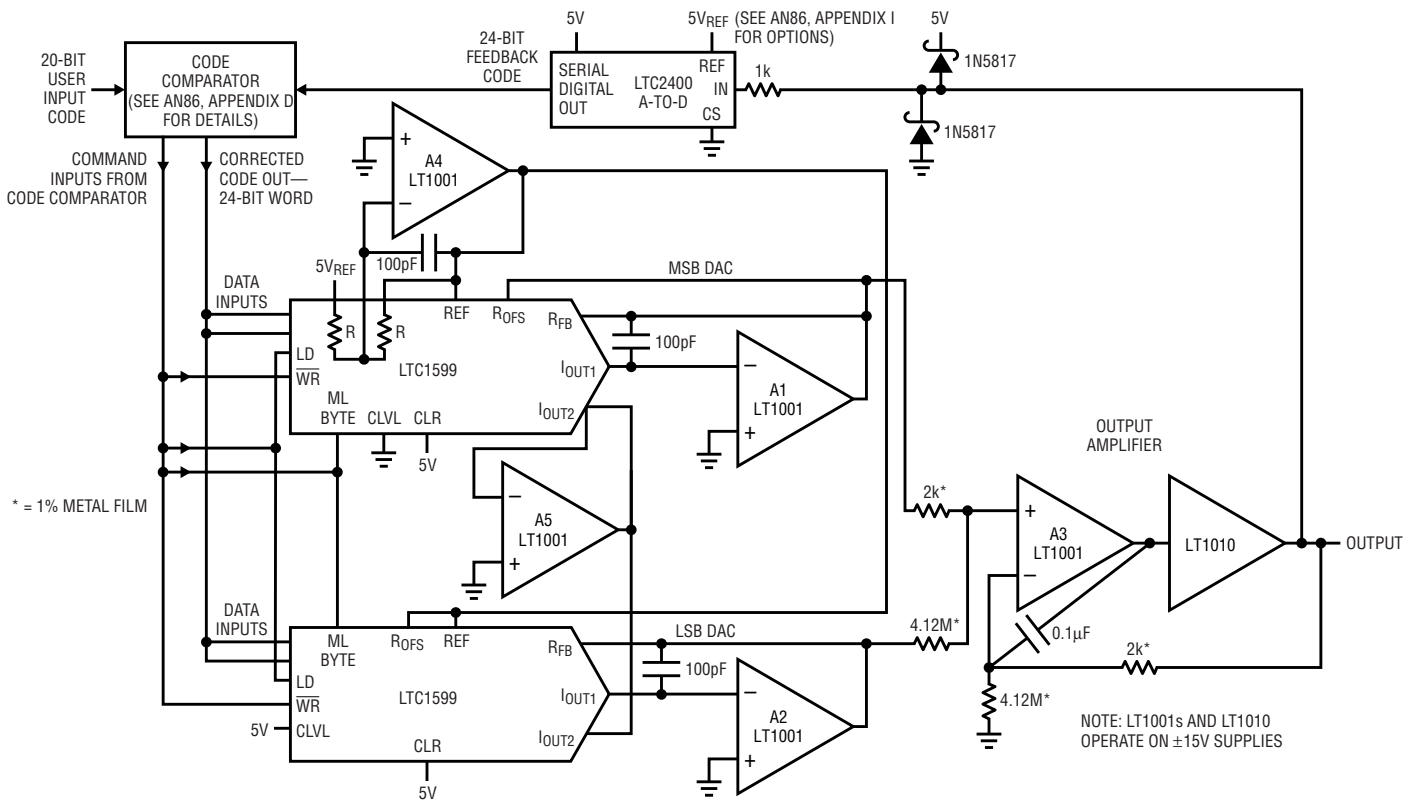


Figure 2. Detail of 1ppm DAC: composite DAC comprises two DAC values summed at the output amplifier. The LTC2400 A-to-D and code comparator furnish stabilizing feedback.

20-Bit DAC, continued from page 1

In practice, the “slave” 20-bit DAC’s output is monitored by the “master” LTC2400 A-to-D, which feeds digital information to a code comparator. The code comparator differences the user input word with the LTC2400 output, presenting a corrected code to the slave DAC. In this fashion, the slave DAC’s drifts and nonlinearity are continuously corrected by the loop to an accuracy determined by the A-to-D converter and V_{REF} .² No other components in the loop need to be stable.

This loop has a number of desirable attributes. As mentioned, accuracy limitations are set by the A-to-D converter and its reference. Additionally, loop behavior averages low order bit indexing and jitter, obviating the loop’s inherent small-signal instability. Finally, classical remote sensing may be used or digitally based sensing is possible by placing the A-to-D converter at the load. The A-to-D’s SO-8 package and lack of external components makes this digitally incarnated Kelvin sensing scheme practical.³

Circuitry Details

Figure 2 is a detailed schematic of the 1ppm DAC. The slave DAC comprises two DACs. The upper 16 bits of the code comparator’s output are fed to a 16-bit DAC (“MSB DAC”), while the lower bits are converted by a separate DAC (“LSB DAC”). Although a total of 32 bits are presented to the two DACs, there are 8 bits of overlap, ensuring loop capture under all conditions. The composite DACs’ resultant 24-bit resolution provides 4 bits of indexing range below the 20th bit, ensuring a

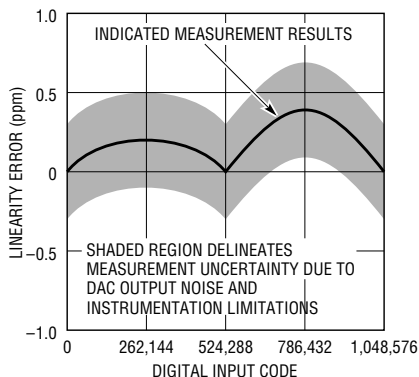


Figure 3. Linearity plot shows no error outside 1ppm for all codes.

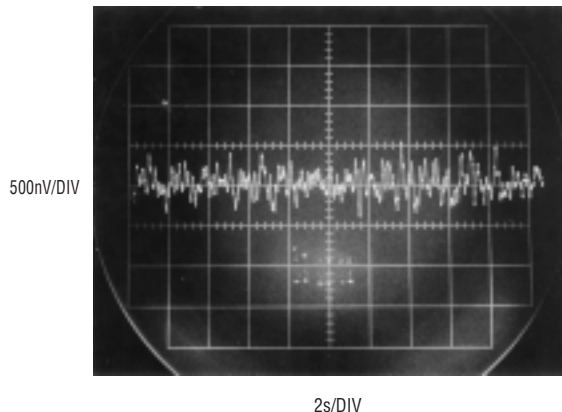


Figure 4. Output noise indicates less than 1µV, about 0.2LSB. The measurement noise floor, due to equipment limitations, is 0.2µV.

stable LSB of 1ppm of scale. A1 and A2 transform the DAC's output currents into voltages, which are summed at A3. A3's scaling is arranged so that the correction loop can always capture and correct any combination of zero- and full-scale errors. A3's output, the circuit output, feeds the LTC2400 A-to-D. The LT1010 provides buffering to drive loads and cables. The A-to-D's digital output is differenced against the input word by the code comparator, which produces a corrected code. This corrected code is applied to the MSB and LSB DACs, closing a feedback loop. The loop's integrity is determined by A-to-D converter and voltage reference errors. The resistor and diodes at the 5V powered A-to-D protect it from inadvertent A3 outputs (power up, transient, lost supply, etc.). A4 is a reference inverter and A5 provides a clean ground potential to both DACs.

Linearity Considerations

A-to-D linearity determines overall DAC linearity. The A-to-D has about ± 2 ppm nonlinearity. In applications where this error is permissible, it may be ignored. If 1ppm linearity is required, it is obtainable by correcting the residual linearity error with software techniques. Details on LTC2400 linearity and this feature are presented in Appendices D and E of AN86.

DC Performance Characteristics

Figure 3 is a plot of linearity vs input code. The data shows linearity is within 1ppm over all codes. Output noise, measured in a 0.1Hz to 10Hz bandpass, is seen in Figure 4 to be about 0.2LSB. This measurement is somewhat corrupted by equipment limitations, which set a noise floor of about 0.2 μ V.

Dynamic Performance

The A-to-D's conversion rate combines with the loop's sampled data characteristic and slow amplifiers to dictate relatively slow DAC response. Figure 5's slew response requires about 150 microseconds.

continued on page 14

 


Figure 5. DAC output full-scale slew characteristics

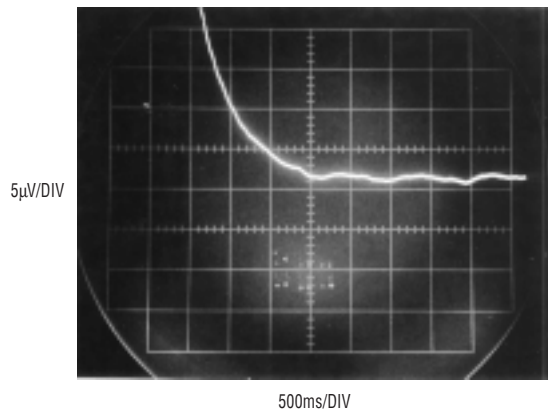


Figure 6. High resolution settling detail after a full-scale step: settling time is 1400 milliseconds to within 1ppm ($\pm 5\mu$ V).

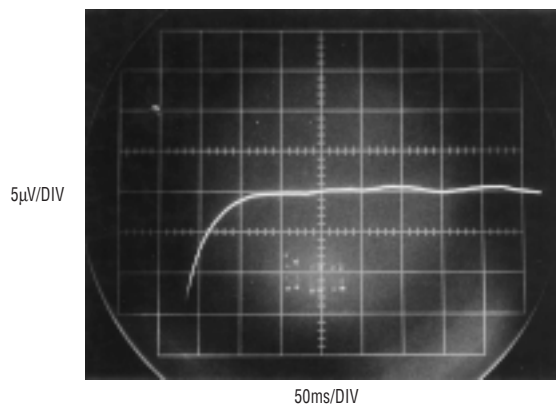



Figure 7. Small-step settling time measures 100 milliseconds to within 1ppm ($\pm 5\mu$ V) for a 500 μ V transition.

20-bit DAC, continued from page 4

Figure 6 shows full-scale DAC settling time to within 1ppm ($\pm 5\mu\text{V}$) requires about 1400 milliseconds. A smaller step (Figure 7) of $500\mu\text{V}$ needs only 100 milliseconds to settle within 1ppm.

Conclusion

Summarized 1ppm DAC specifications appear in Table 1. These specifications should be considered guidelines, as the options and variations noted will affect performance. Consult the appropriate appendices of LTC Application Note 86 for design specifics and trade-offs. 

1. This article is excerpted from Linear Technology Application Note 86, *A Standards Lab Grade 20-Bit DAC with 0.1ppm/ $^{\circ}\text{C}$ Drift*. Considerably more detail is available in that publication.
2. D-to-A converters have been placed in loops to make A-to-D converters for a long time. Here, an A-to-D converter feeds back a loop to form a D-to-A converter. There seems a certain justified symmetry to this development. Turnabout is indeed fair play.
3. One wonders what Lord Kelvin's response would be to the digitization of his progeny. Such uncertainties are the residue of progress.

Table 1. Summarized specifications for the 20-bit DAC

Parameter	Specification
Resolution	1ppm
Full-Scale Error	4ppm of V_{REF} (Trimmable to 1ppm by V_{REF} Adjustment)
Full-Scale Error Drift	0.04ppm/ $^{\circ}\text{C}$ Exclusive of Reference (0.1ppm/ $^{\circ}\text{C}$ with LTZ1000A Reference) See Note 4
Offset Error	0.5ppm
Offset Error Drift	0.01ppm/ $^{\circ}\text{C}$
Nonlinearity	± 2 ppm, Trimmable to Less Than 1ppm See Note 5
Output Noise	0.2ppm ($\approx 0.9\mu\text{V}$, 0.1Hz to 10Hz BW)
Slew Rate	0.033V/ μs
Settling Time—Full-Scale Step	1400 Milliseconds
Settling Time— $500\mu\text{V}$ Step	100 Milliseconds
Output Voltage Range	0V to 5V. For Other Ranges See Note 6
Note 4: See AN 86, Appendix I Note 5: See AN 86, Appendix E Note 6: See AN 86, Appendices E and F	